



INSTITUTE OF ENGINEERING CENTRAL CAMPUS, PULCHOWK

FILTER DESIGN

LAB #3

COMPARISON OF MAGNITUDE & PHASE RESPONSE OF DIFFERENT FILTERS

Submitted BY:
AMRIT PRASAD PHUYAL
Roll: PULL074BEX004

Submitted To:
SHARAD KUMAR GHIMIRE
Department of Electronics and
Computer Engineering

July 31, 2021

Table of Contents

1 Title 1

2 Objective 1

3 Requirement 1

3.1 Proteus Design Suite 1

4 Theory 1

4.1 Butterworth Filter 1

4.2 Chebyshev Filter 2

4.3 Bessel Filter 3

5 Exercises: 4

5.1 Question -1 4

5.2 Question -2 8

5.3 Question -3 12

5.4 Question -4 14

6 Discussion & Conclusion 18

List of Figures

1	Frequency response off Butterworth filter for various order	1
2	Frequency response of Chebyshev I filter	2
3	Frequency response of Chebyshev II (Inverse) filter	3
4	Frequency response of Bessel filter	3
5	Third order Butterworth Filter at half power frequency ($\omega_0 = 1$ rad/sec)	4
6	Butterworth Filter at half power frequency ($\omega_0 = 10000$ rad/sec)	5
7	Proteus Circuit Figure a	5
8	Proteus Observation Figure a	6
9	Output signal for input square wave of 100Hz	6
10	Output signal for input square wave of 1.6kHz	7
11	Output signal for input square wave of 3.2kHz	7
12	Output signal for input square wave of 5kHz	8
13	Chebyshev having passband frequency of 1 rad/sec and 1 dB ripple	8
14	Chebyshev having passband frequency of 1000 rad/sec and 1 dB ripple	9
15	Proteus Circuit Figure b	9
16	Proteus Observation Figure b	10
17	Output signal for input square wave of 100Hz	10
18	Output signal for input square wave of 1.6kHz	11
19	Output signal for input square wave of 3.2kHz	11
20	Output signal for input square wave of 5kHz	12
21	Chebyshev having passband frequency of 1 rad/sec and 3dB ripple	12
22	Chebyshev having passband frequency of 1000 rad/sec and 3 dB ripple	13
23	Proteus Circuit Figure c	13
24	Proteus Observation Figure c	14
25	Bessel filter at normalized frequency of 1 rad/sec	15
26	Bessel filter at normalized frequency of 1000 rad/sec	15
27	Proteus Circuit Figure d	16
28	Proteus Observation Figure d	16
29	Output signal for input square wave of 100Hz	17
30	Output signal for input square wave of 1.6kHz	17
31	Output signal for input square wave of 3.2kHz	18
32	Output signal for input square wave of 5kHz	18

1 Title

COMPARISON OF MAGNITUDE & PHASE RESPONSE OF DIFFERENT FILTERS

2 Objective

- To design Butterworth, Chebyshev and Bessel filters
- To observe and compare the magnitude and phase response of different filters

3 Requirement

3.1 Proteus Design Suite

Proteus is a simulation and design software tool developed by Labcenter Electronics for Electrical and Electronic circuit design. It is used to create schematic of a circuit and Visualization of its operation.

4 Theory

4.1 Butterworth Filter

Butterworth Filter is signal processing filter designed in such a way that the passband has flat frequency response and roll-offs towards zero in stopband. Frequency response of Butterworth filter having halfpower frequency (ω) is given by

$$|H(w)| = \frac{1}{\sqrt{1 + (\frac{w}{w_0})^{2n}}}$$

Here, n is order of Butterworth Filter.

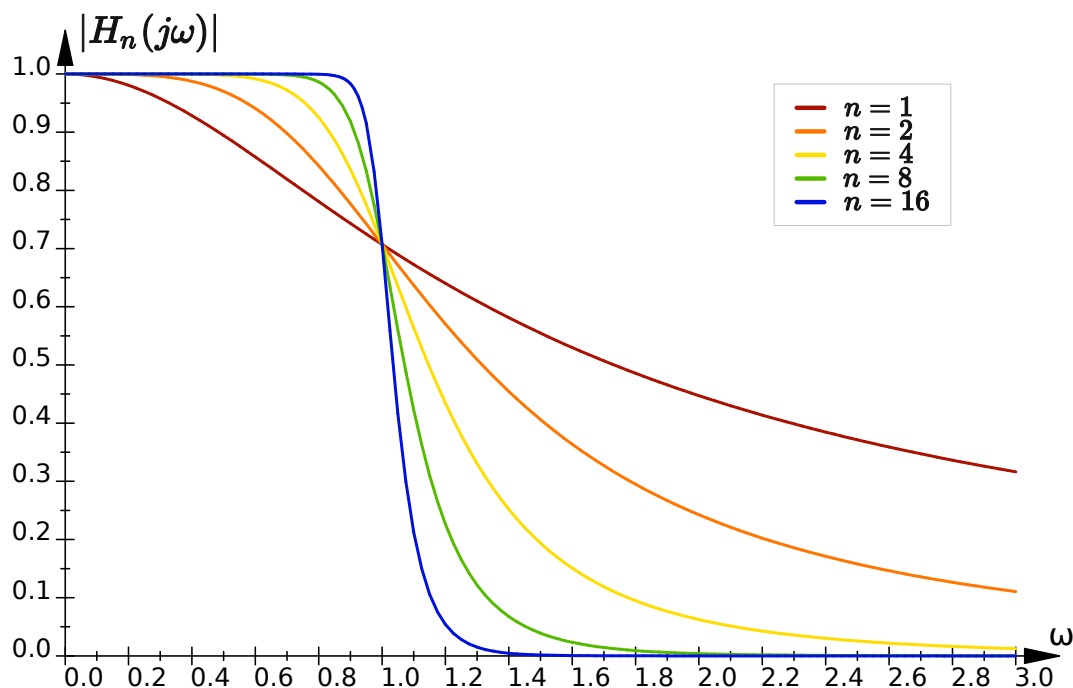


Figure 1: Frequency response off Butterworth filter for various order

4.2 Chebyshev Filter

Chebyshev Filter is signal processing filter designed in such a way that transition band has steeper frequency response than Butterworth filter. There are two types of Chebyshev filters. Type I (Chebyshev) has ripple only in Passband and Type II (Inverse Chebyshev) has ripple only in Stopband. For Chebyshev Filter of order n , the frequency response is given by:

$$|T(j\omega)|^2 = \frac{1}{1 + \epsilon^2 C_n^2(\omega)}$$

where $C_n(\omega)$ is the Chebyshev polynomial of order n .

$$C_n(\omega) = \begin{cases} \cos(n \cos^{-1} \omega), & 0 \leq \omega \leq 1 \\ \cosh(n \cosh^{-1} \omega), & \omega \geq 1 \end{cases}$$

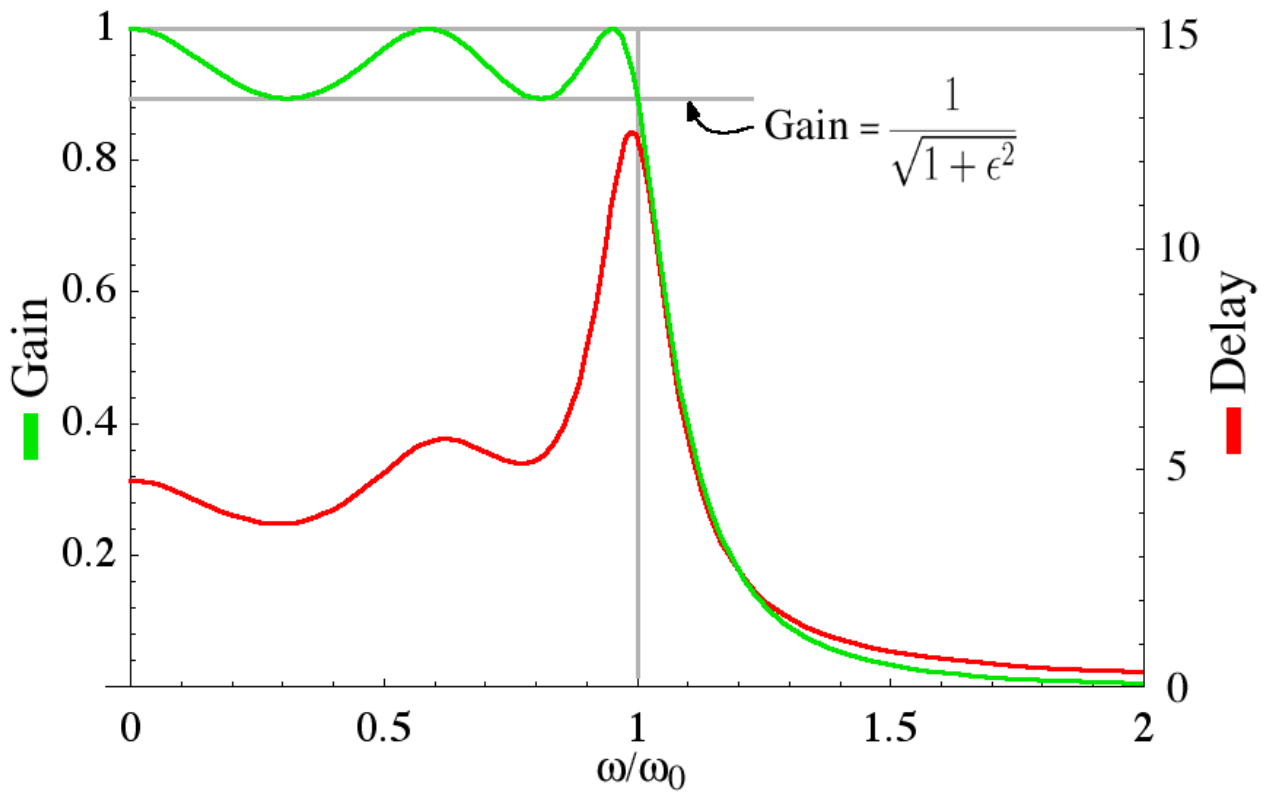


Figure 2: Frequency response of Chebyshev I filter

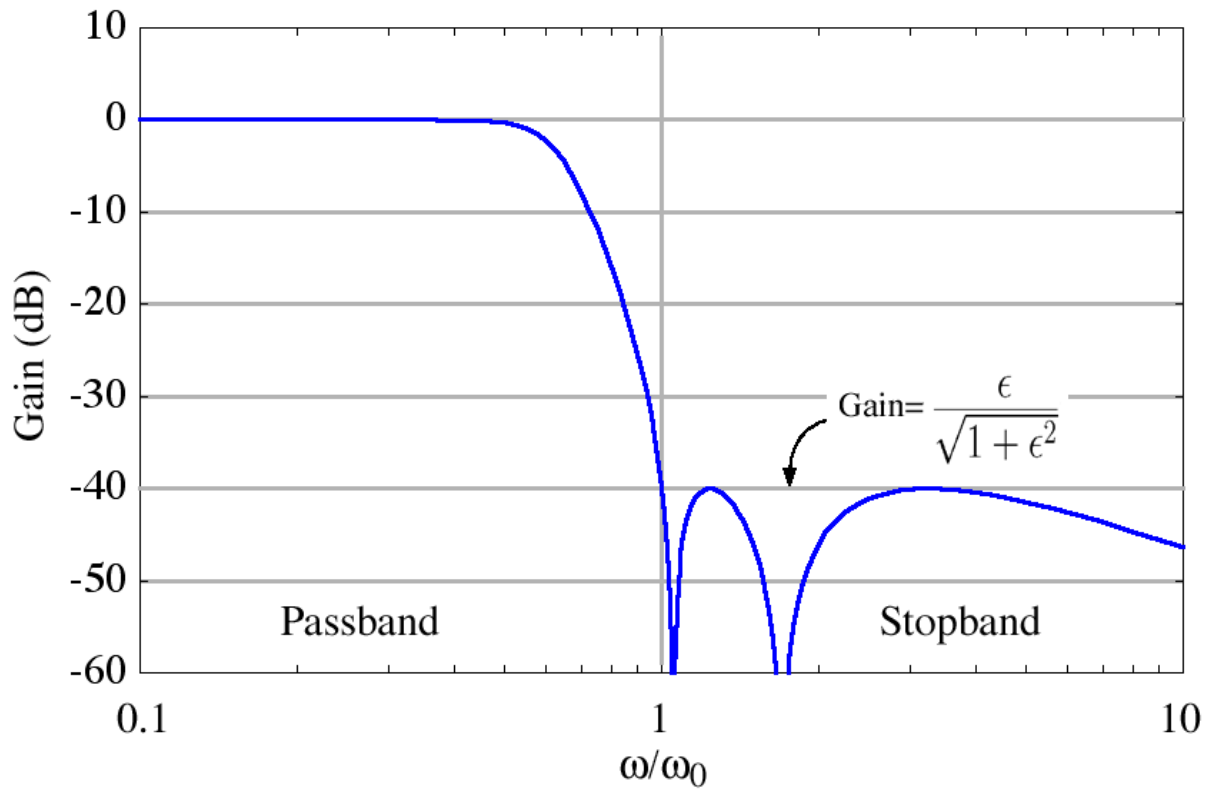


Figure 3: Frequency response of Chebyshev II (Inverse) filter

4.3 Bessel Filter

Bessel Filter is signal processing filter designed to provide a constant group delay in passband thus preserving the wave shape and generally used in audio crossover system. It's frequency response is given by:

$$T_n(s) = \frac{\theta_n(0)}{\theta_n(s/w_0)}$$

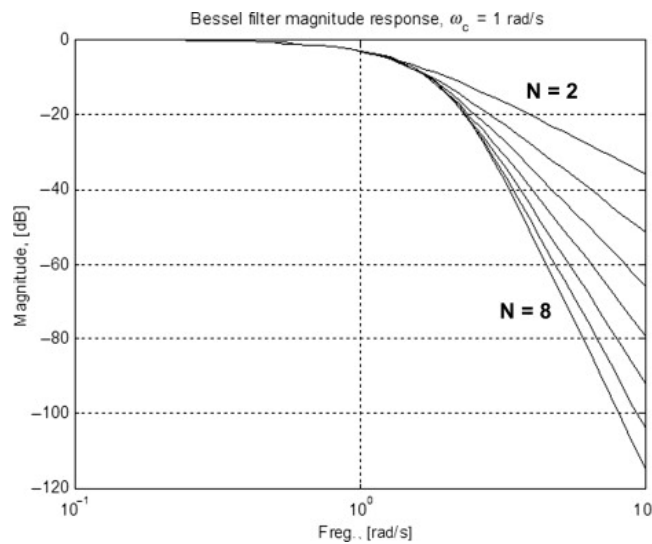


Figure 4: Frequency response of Bessel filter

5 Exercises:

5.1 Question -1

The circuit given in figure 1 below is a Butterworth low-pass filter having half power frequency of 1 rad/sec. From this circuit design a lowpass filter having half power frequency of 10000 rad/sec and practically realizable elements. Realize the circuit, observe and plot the magnitude as well as phase response. Also show the highest gain in dB and half power frequency in your plot.

Observe the output in the oscilloscope when a square wave of 100 Hz is applied at input. Observe the output by increasing frequency upto 5 KHz. Comment on the result.

Typically note down the output when the square wave around 1.6 KHz is applied at input.

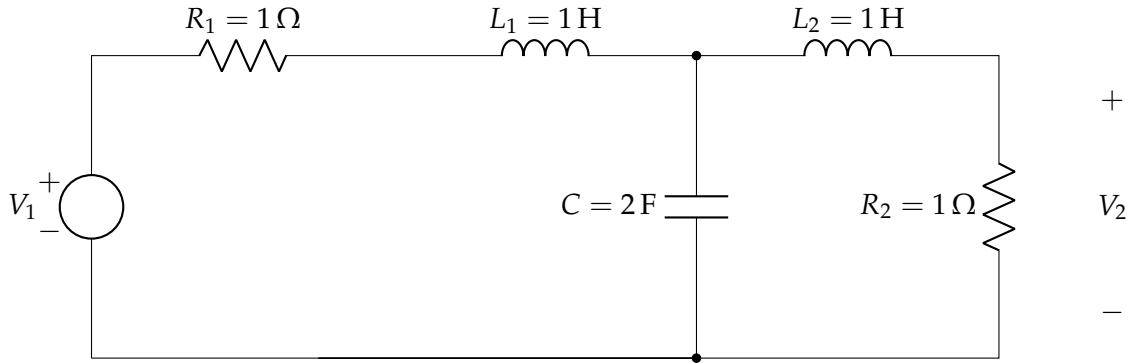


Figure 5: Third order Butterworth Filter at half power frequency ($\omega_0 = 1$ rad/sec)

Given,

Half power frequency of normalized filter (ω_0) = 1 rad/sec

Required half power frequency (ω) = 10000 rad/sec

$$k_f = \frac{(\omega)}{(\omega_0)} = \frac{10000}{1} = 10000$$

To make filter practically realizable we consider Impedance scaling K_m be 500

$$R_{new} = K_m \cdot R_{old} = 500 * 1 = 500 \Omega$$

$$\rightarrow R_1 = R_2 = 500 \Omega$$

$$L_{new} = \frac{K_m}{K_f} L_{old} = \frac{500}{10000} * 1 = 0.05 \text{ H}$$

$$\rightarrow L_1 = L_2 = 0.05 \text{ H} = 50 \text{ mH}$$

$$C_{new} = \frac{1}{K_m \cdot K_f} C_{old} = \frac{1}{500 * 10000} * 2 = 4 * 10^{-7} \text{ F}$$

$$\rightarrow C = 4 * 10^{-7} \text{ F} = 0.4 \mu\text{F}$$

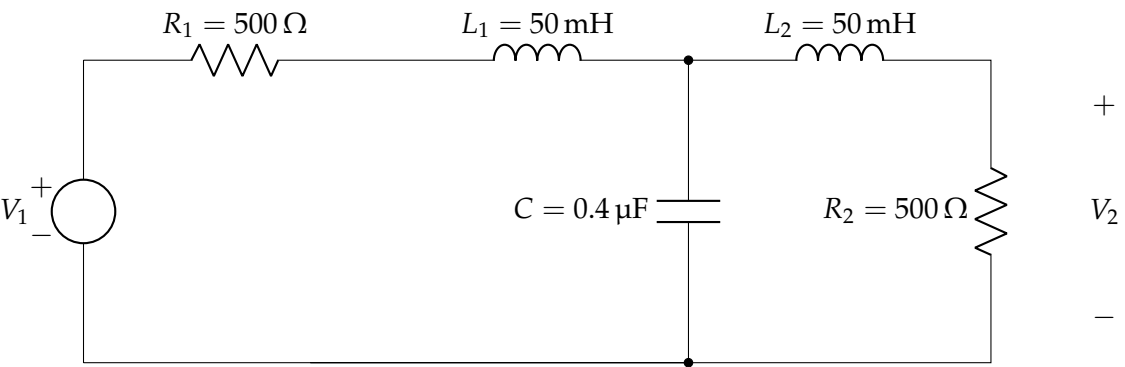


Figure 6: Butterworth Filter at half power frequency ($\omega_0 = 10000\text{ rad/sec}$)

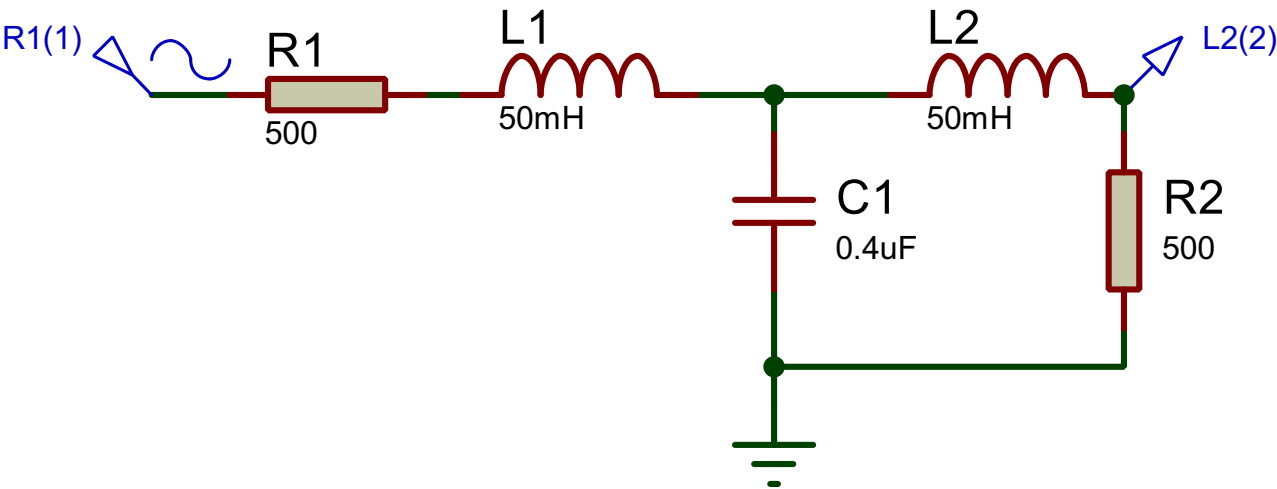


Figure 7: Proteus Circuit Figure a

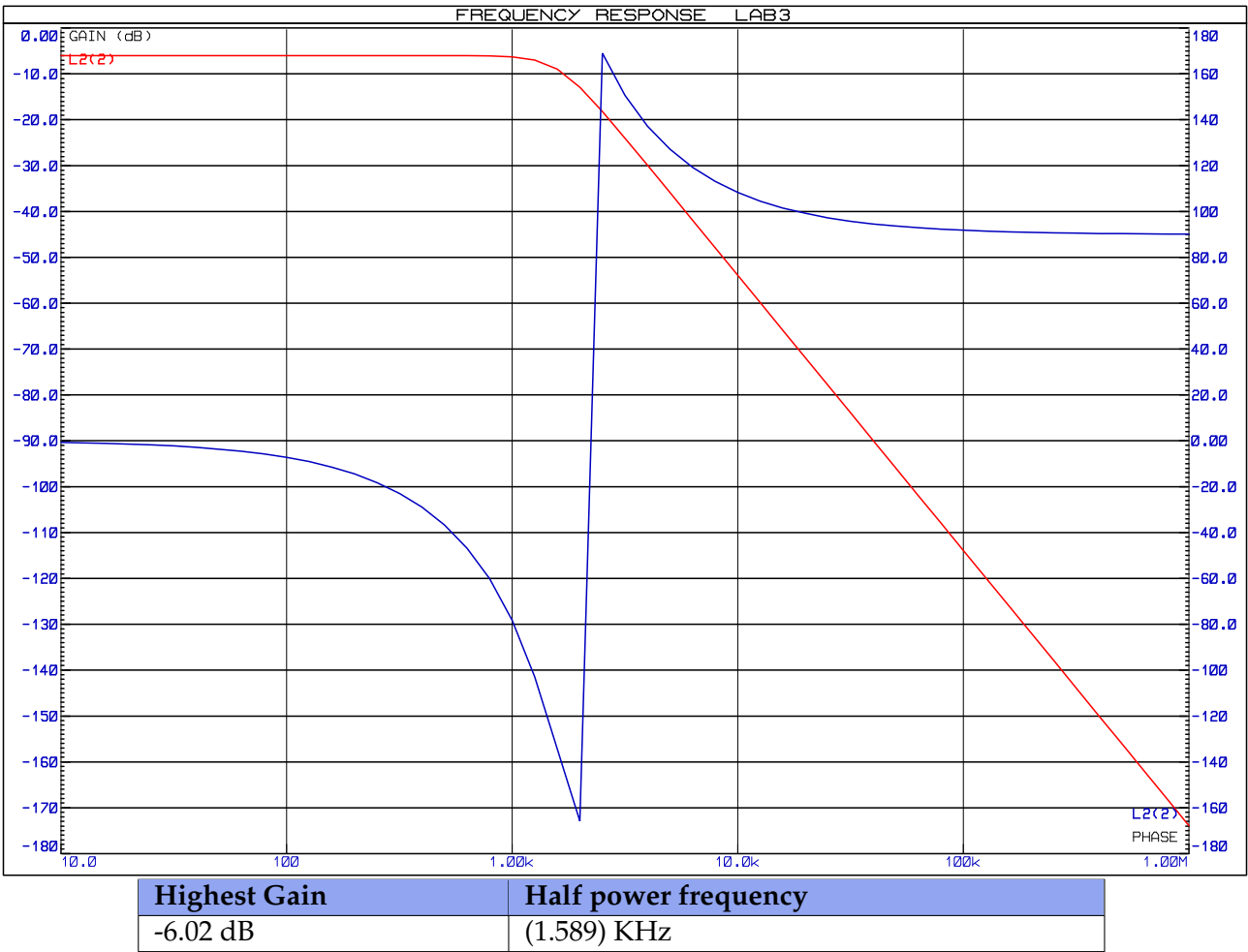


Figure 8: Proteus Observation Figure a

No ripple is seen in Passband and transtion is gradual till stopband.

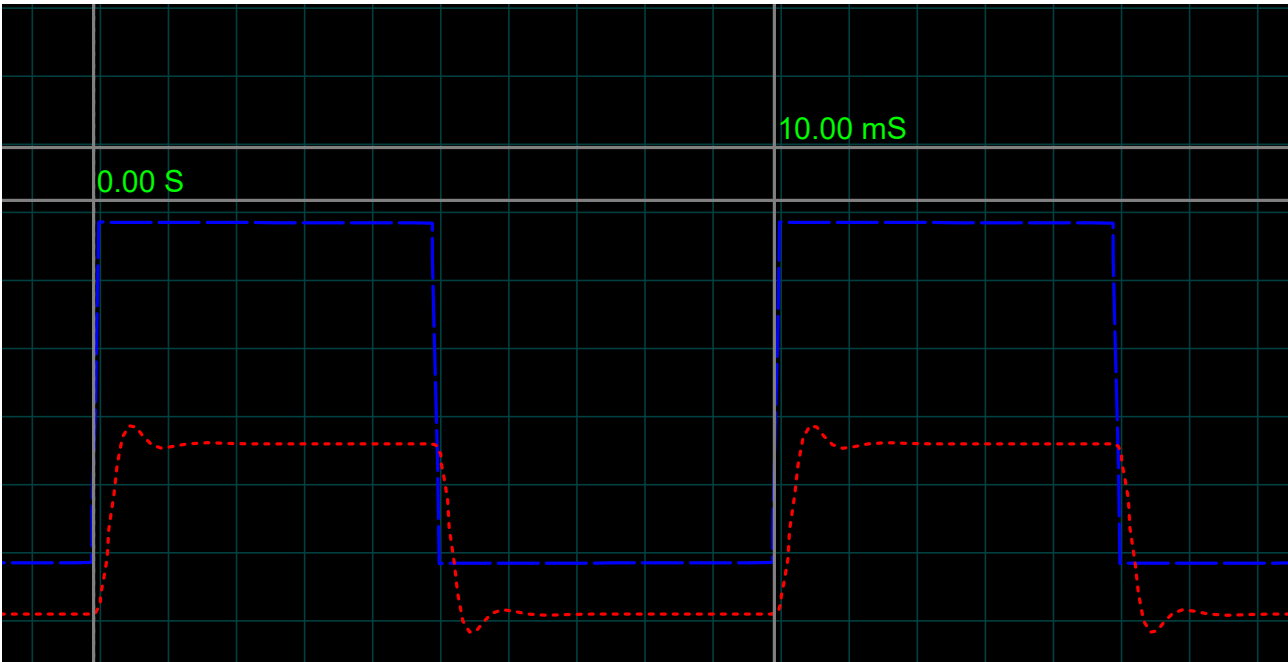


Figure 9: Output signal for input square wave of 100Hz

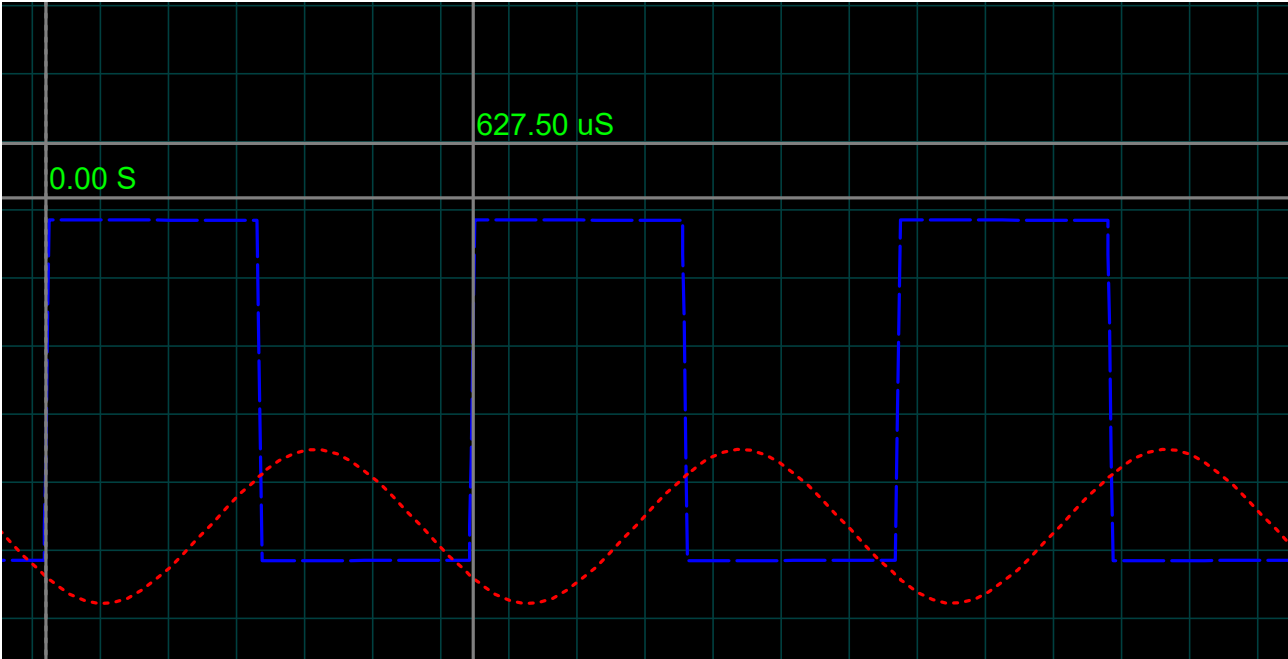


Figure 10: Output signal for input square wave of 1.6kHz

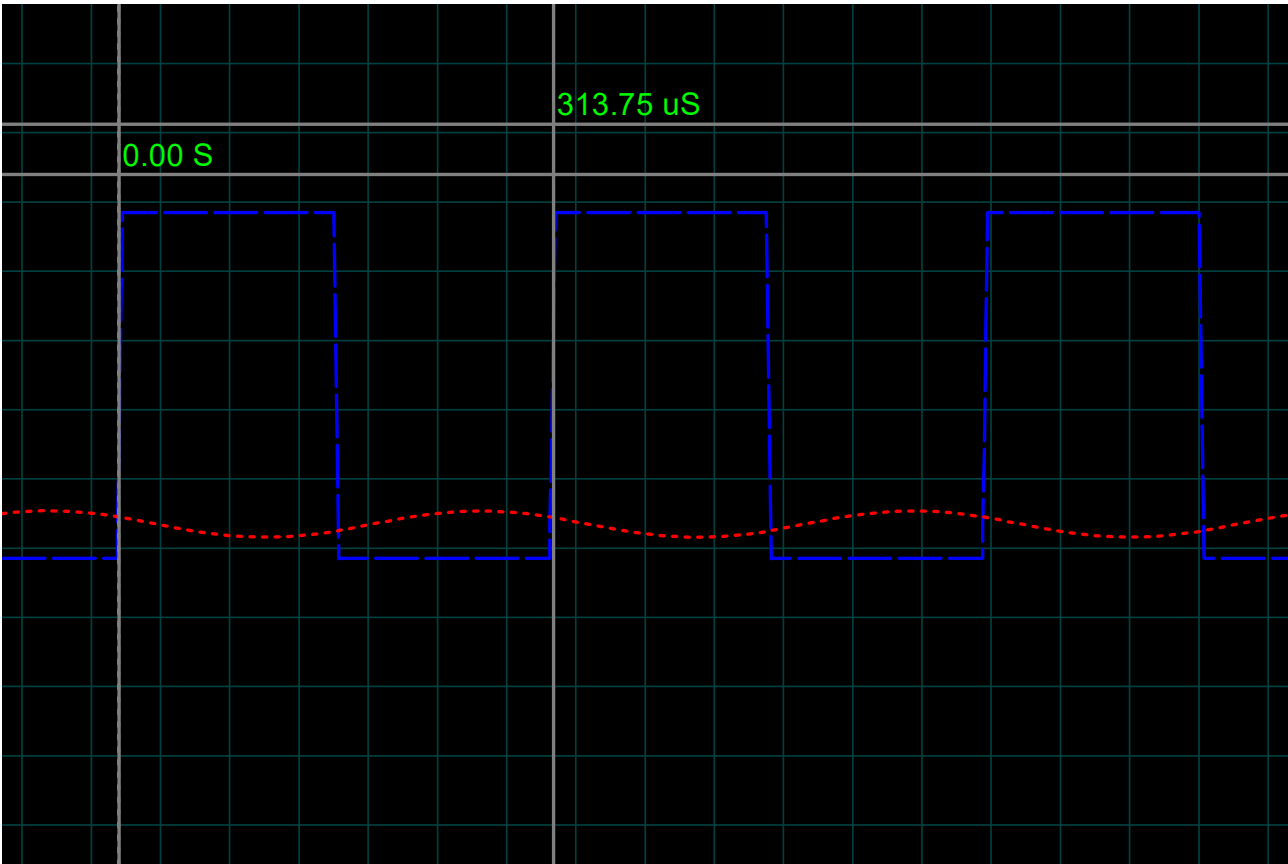


Figure 11: Output signal for input square wave of 3.2kHz

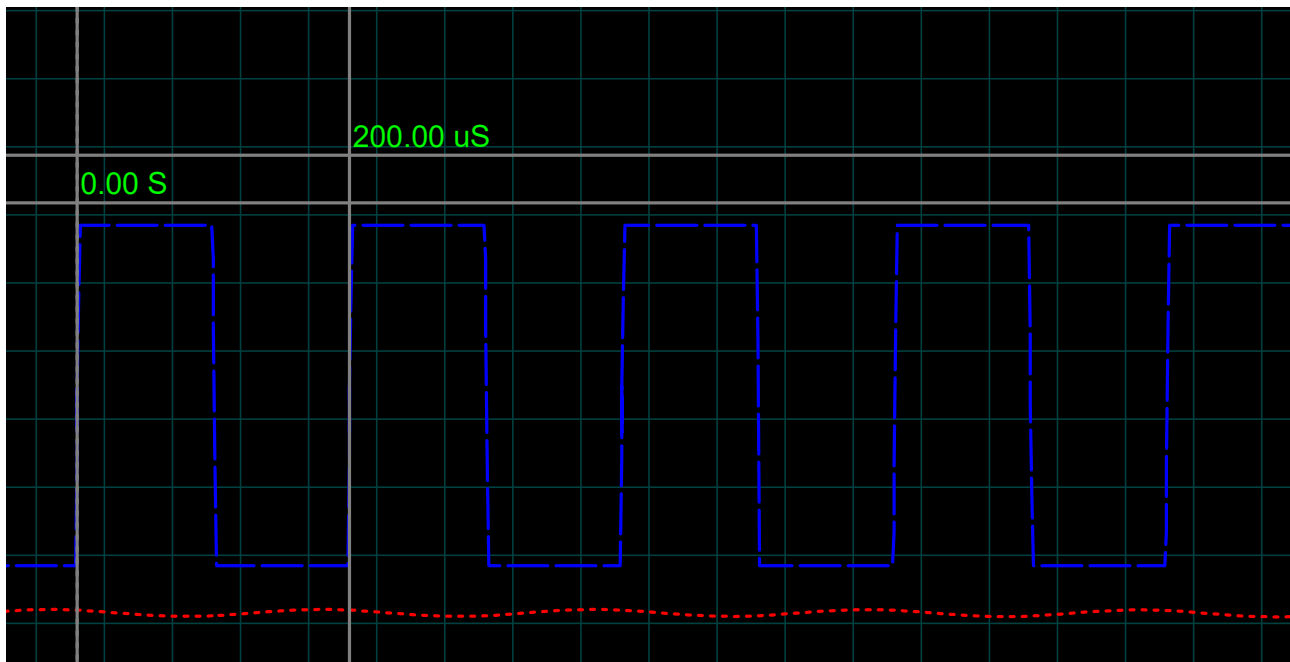


Figure 12: Output signal for input square wave of 5kHz

In above observation , in 100 Hz spikes is seen near the edges . As the frequency increases and reached 1.6kHz sine wave is seen in the middle. From 3.2 khz to 5.0 khz , the output is getting smother.

5.2 Question -2

The circuit given in figure 2 below is a low-pass Chebyshev filter having passband frequency of 1 rad/sec and attenuation of 1dB. From this circuit design a lowpass filter having passband frequency of 10000 rad/sec and practically realizable elements. Realize the circuit, observe and plot the magnitude as well as phase response. Also show the highest gain in dB and half power frequency in your plot. Note down the ripple within the entire passband.

Observe the output in oscilloscope when square wave of 100 Hz is applied at input. Observe the output by increasing frequency upto 5 KHz. Comment on the result.

Typically note down the output when square wave around 1.6 KHz is applied at input.

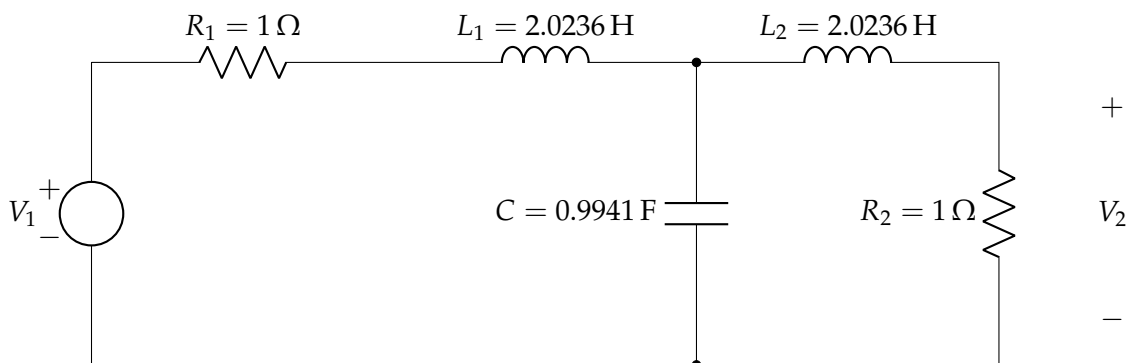


Figure 13: Chebyshev having passband frequency of 1 rad/sec and 1 dB ripple

Given,

Half power frequency of normalized filter (ω_0) = 1 rad/sec

Required half power frequency (ω)= 10000 rad/sec

$$k_f = \frac{(\omega)}{(\omega_0)} = \frac{10000}{1} = 10000$$

To make filter practically realizable we consider Impedance scaling K_m be 500

$$R_{new} = K_m \cdot R_{old} = 500 \cdot 1 = 500\Omega$$

$$\rightarrow R_1 = R_2 = 500\Omega$$

$$L_{new} = \frac{K_m}{K_f} L_{old} = \frac{500}{10000} \cdot 2.0236 = 0.10118 \text{ H}$$

$$\rightarrow L_1 = L_2 = 0.10118 \text{ H} = 101.18 \text{ mH}$$

$$C_{new} = \frac{1}{K_m \cdot K_f} C_{old} = \frac{1}{500 \cdot 10000} \cdot 0.9941 = 1.9882 \cdot 10^{-7} \text{ F}$$

$$\rightarrow C = 1.9882 \cdot 10^{-7} \text{ F} = 0.19882 \mu\text{F}$$

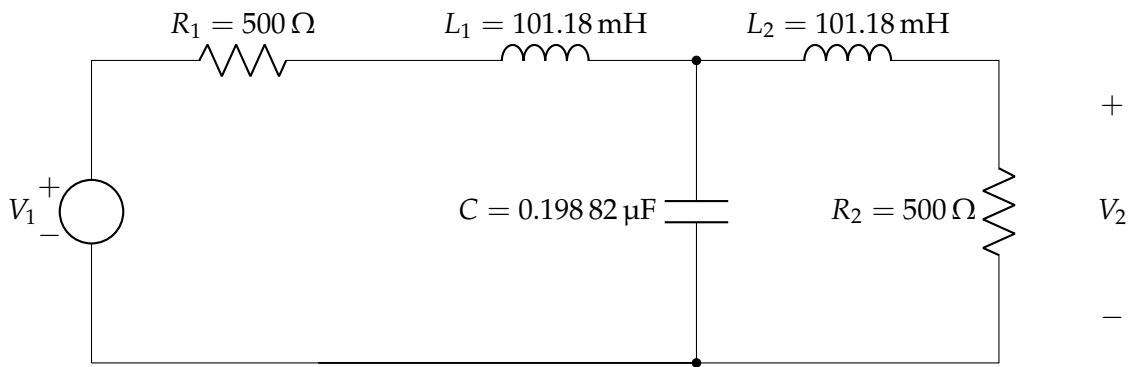


Figure 14: Chebyshev having passband frequency of 1000 rad/sec and 1 dB ripple

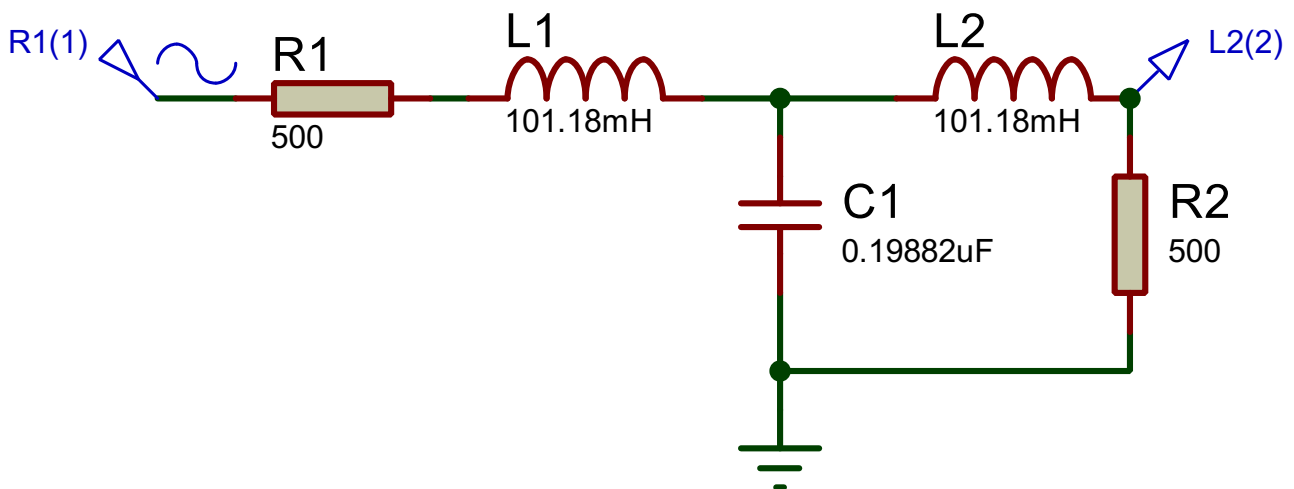


Figure 15: Proteus Circuit Figure b

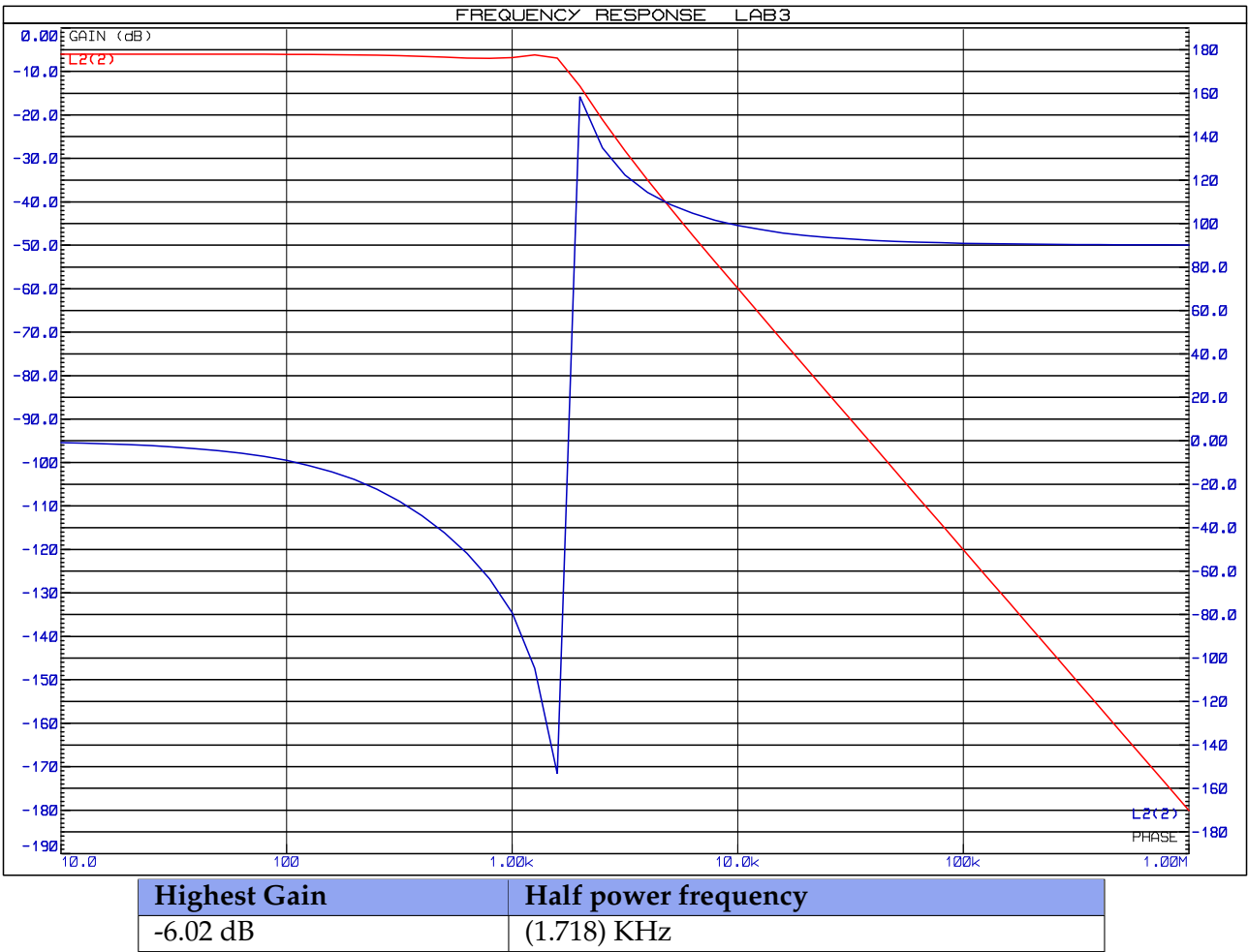


Figure 16: Proteus Observation Figure b

Lowest ripple = -7.02 dB thus ripple in the passband = 1 dB

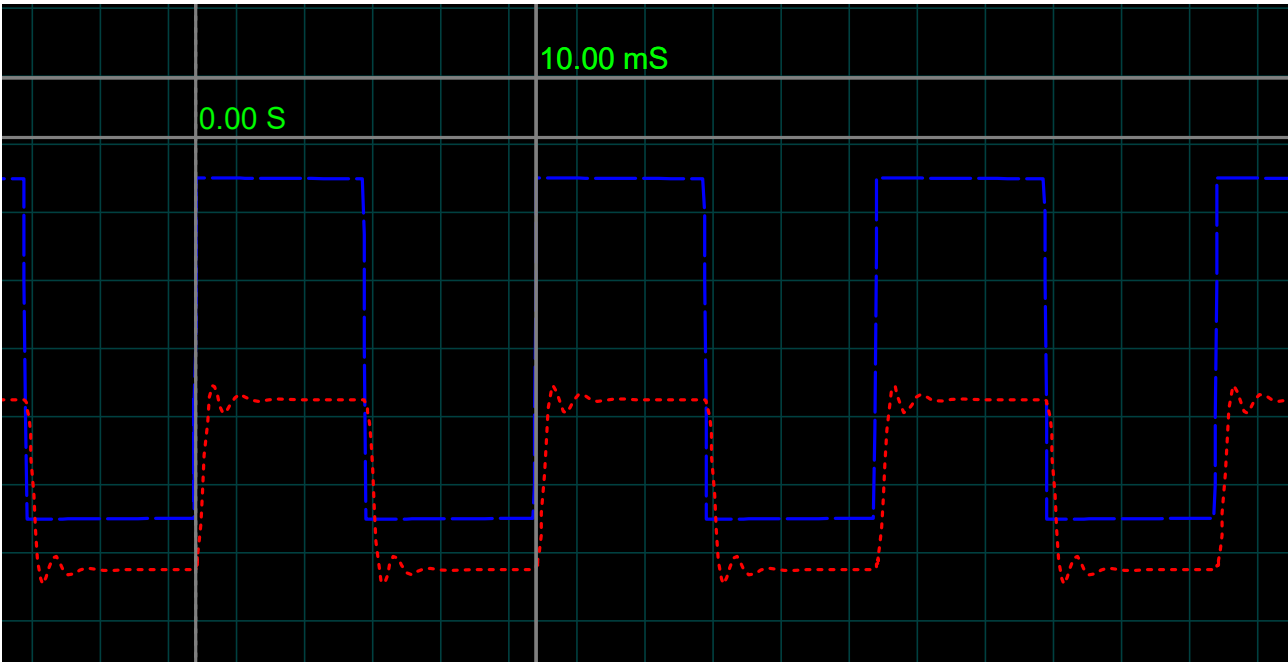


Figure 17: Output signal for input square wave of 100Hz

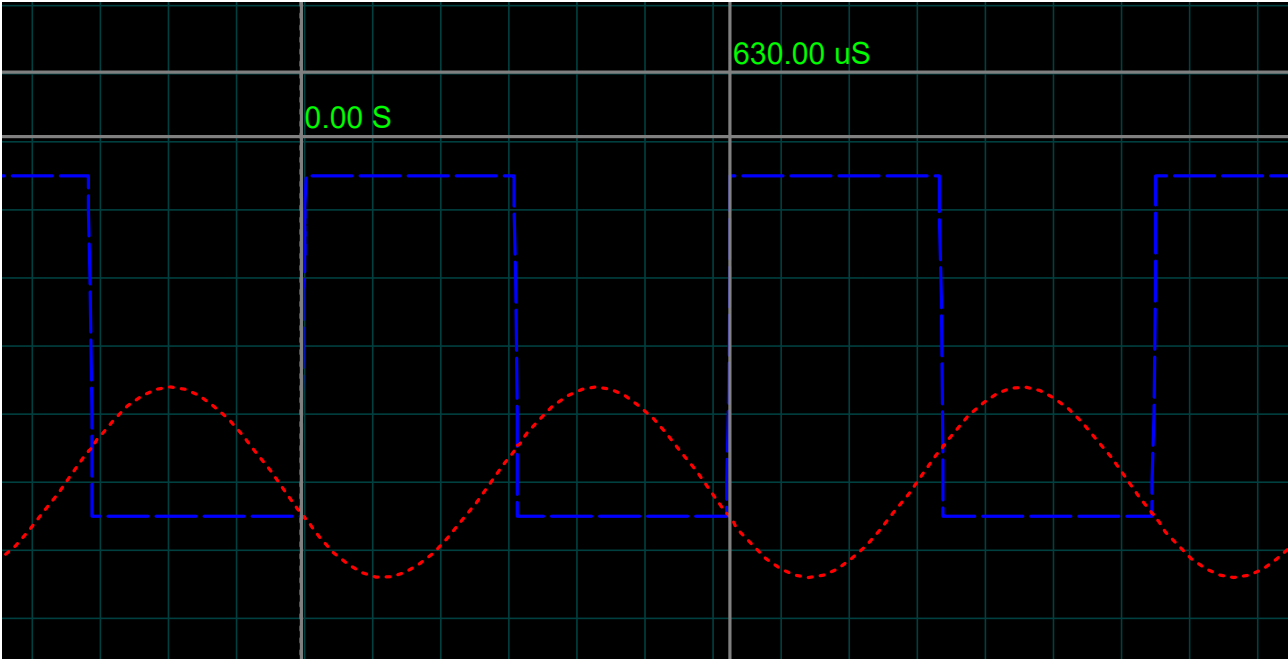


Figure 18: Output signal for input square wave of 1.6kHz

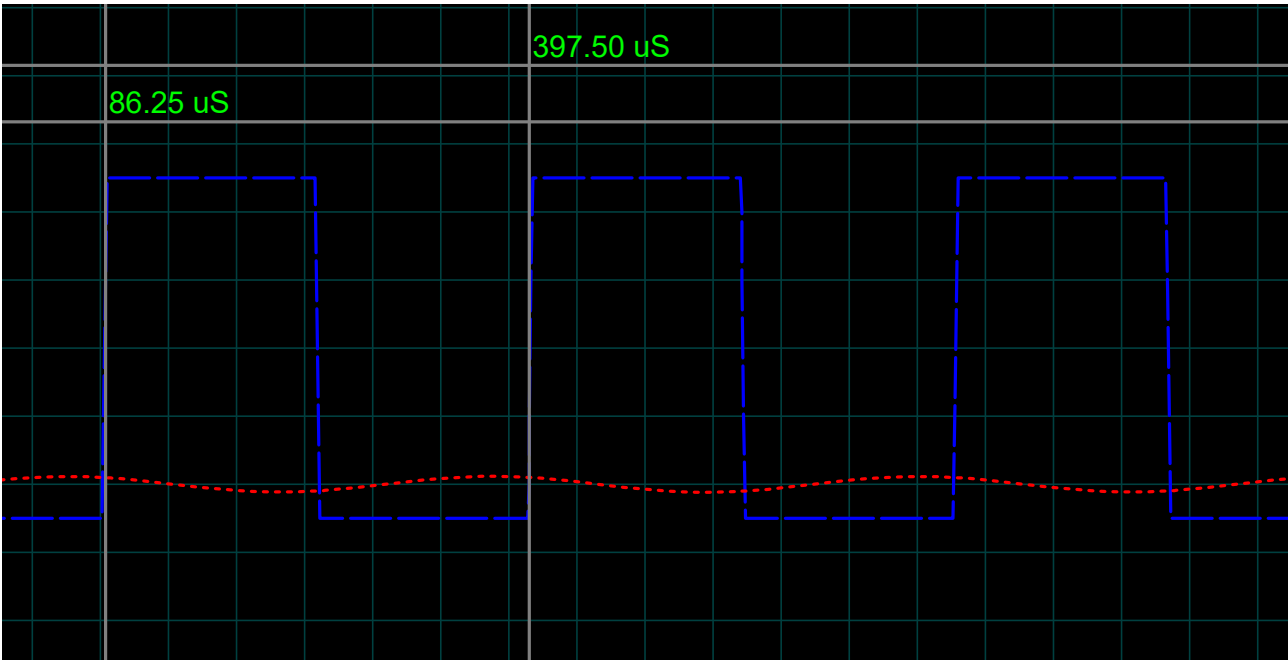


Figure 19: Output signal for input square wave of 3.2kHz

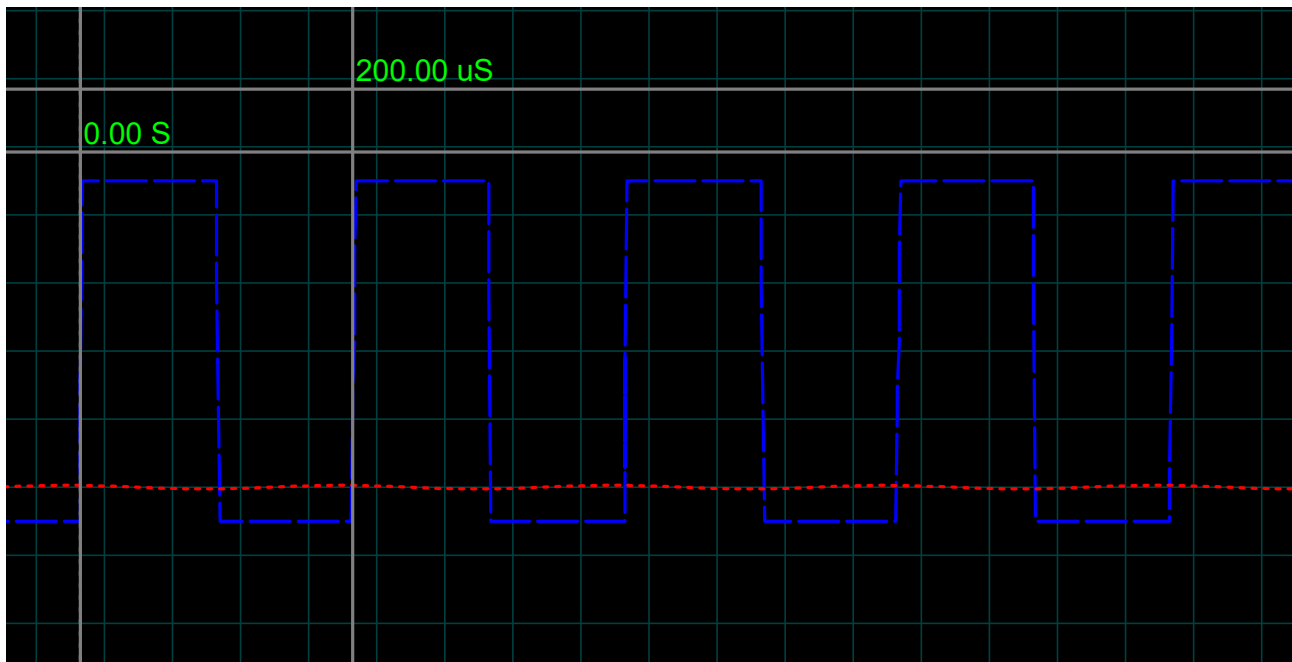


Figure 20: Output signal for input square wave of 5kHz

In above observation , in 100 Hz spikes is seen near the edges . As the frequency increases and reached 1.6kHz sine wave is seen in the middle. From 3.2 khz to 5.0 khz , the output is getting smother.

5.3 Question -3

Let us modify the elements as shown in figure 3 below to have the Chebyshev lowpass filter with 3 dB ripple. From this circuit design a lowpass filter having passband frequency of 10000 rad/sec and practically realizable elements. Realize the circuit, observe and plot the magnitude as well as phase response. Also show the highest gain in dB and half power frequency in your plot. Note down the ripple within the entire passband. Compare the response with that of problem B.

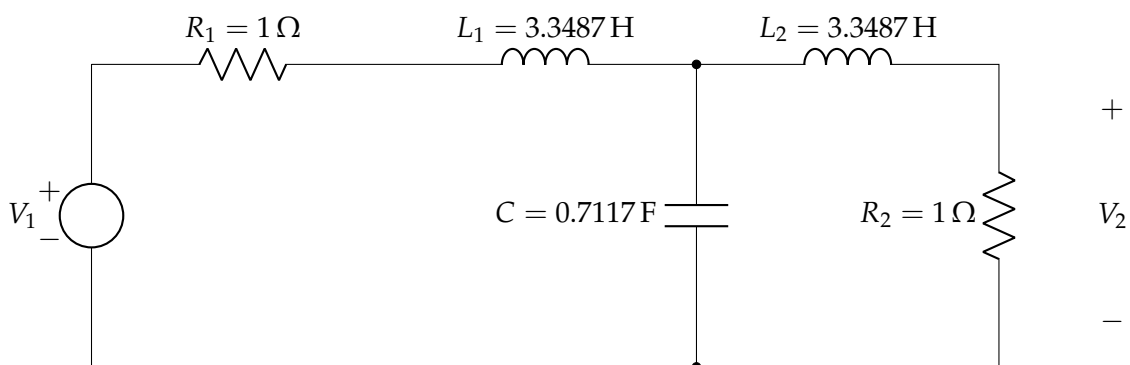


Figure 21: Chebyshev having passband frequency of 1 rad/sec and 3dB ripple

Given,

Half power frequency of normalized filter (ω_0) = 1 rad/sec

Required half power frequency (ω) = 10000 rad/sec

$$k_f = \frac{(\omega)}{(\omega_0)} = \frac{10000}{1} = 10000$$

To make filter practically realizable we consider Impedance scaling K_m be 500

$$R_{new} = K_m \cdot R_{old} = 500 * 1 = 500 \Omega$$

$$\rightarrow R_1 = R_2 = 500 \Omega$$

$$L_{new} = \frac{K_m}{K_f} L_{old} = \frac{500}{10000} * 3.3487 = 0.167435 \text{ H}$$

$$\rightarrow L_1 = L_2 = 0.167435 \text{ H} = 167.435 \text{ mH}$$

$$C_{new} = \frac{1}{K_m \cdot K_f} C_{old} = \frac{1}{500 * 10000} * 0.7117 = 1.4234 * 10^{-7} \text{ F}$$

$$\rightarrow C = 1.4234 * 10^{-7} \text{ F} = 0.14234 \mu\text{F}$$

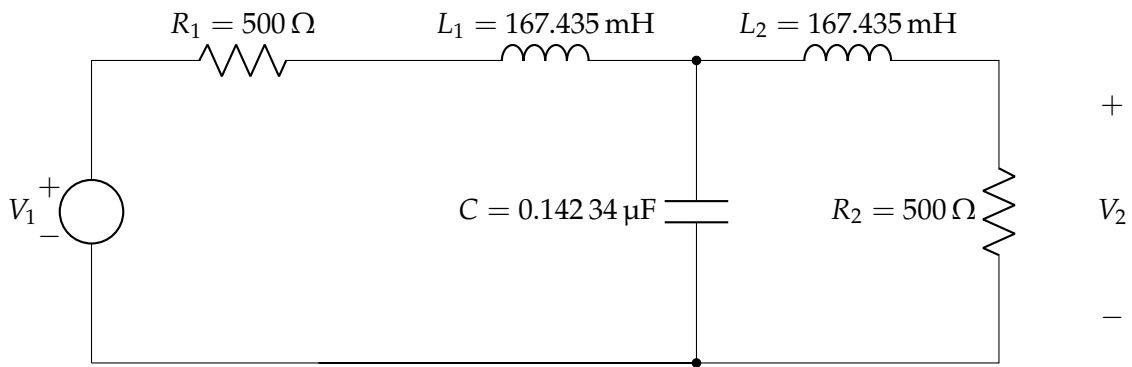


Figure 22: Chebyshev having passband frequency of 1000 rad/sec and 3 dB ripple

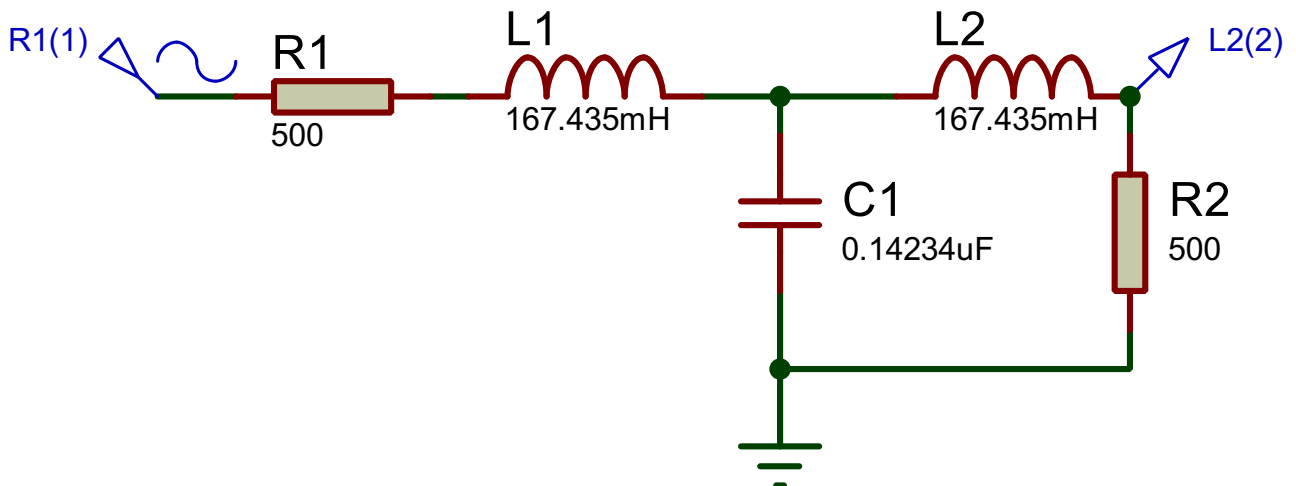


Figure 23: Proteus Circuit Figure c

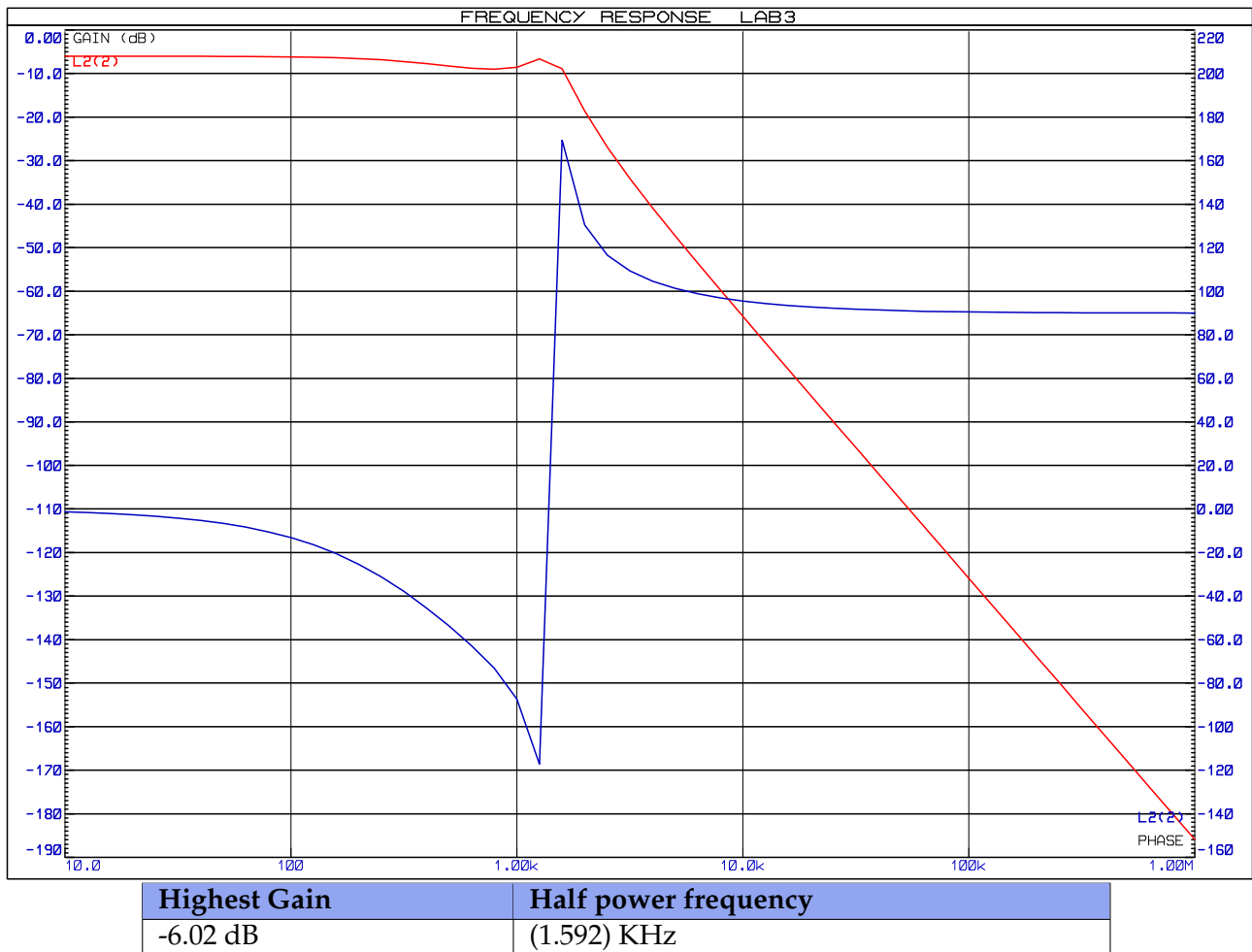


Figure 24: Proteus Observation Figure c

Lowest ripple= -9.02 dB thus ripple in pass band is 3 dB.

Compared to Problem 2 sharper transition is seen in Problem 3.

5.4 Question -4

The circuit given in figure 4 below is a low-pass Bessel filter with normalized frequency. From this circuit design a lowpass filter for the frequency of 10000 rad/sec. All the elements of your final design should be practically realizable. Realize the circuit, observe and plot the magnitude as well as phase response. Also show the highest gain in dB and half power frequency in your plot.

Observe the output in oscilloscope when square wave of 100 Hz is applied at input. Observe the output by increasing frequency upto 5 KHz. Comment on the result.

Typically note down the output when the square wave around 1.6 KHz is applied at input.

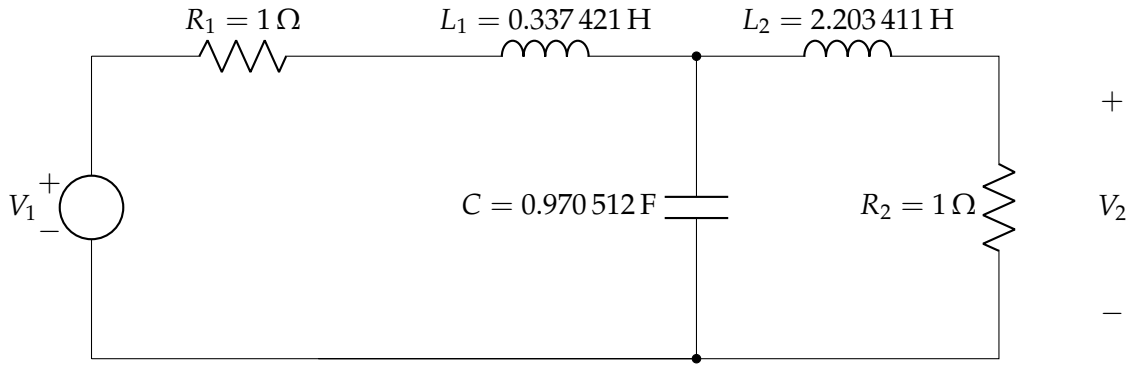


Figure 25: Bessel filter at normalized frequency of 1 rad/sec

Given,

Half power frequency of normalized filter (ω_0) = 1 rad/sec

Required half power frequency (ω) = 10000 rad/sec

$$k_f = \frac{(\omega)}{(\omega_0)} = \frac{10000}{1} = 10000$$

To make filter practically realizable we consider Impedance scaling K_m be 500

$$R_{new} = K_m \cdot R_{old} = 500 * 1 = 500 \Omega$$

$$\rightarrow R_1 = R_2 = 500 \Omega$$

$$L_{new} = \frac{K_m}{K_f} L_{old}$$

$$\rightarrow L_1 = \frac{500}{10000} * 0.337421 = 0.01687105 \text{ H} = 16.87105 \text{ mH}$$

$$\rightarrow L_2 = \frac{500}{10000} * 2.203411 = 0.11017055 \text{ H} = 110.17055 \text{ mH}$$

$$C_{new} = \frac{1}{K_m \cdot K_f} C_{old} = \frac{1}{500 * 10000} * 0.970512 = 1.941024 * 10^{-7} \text{ F}$$

$$\rightarrow C = 1.941024 * 10^{-7} \text{ F} = 0.1941024 \mu\text{F}$$

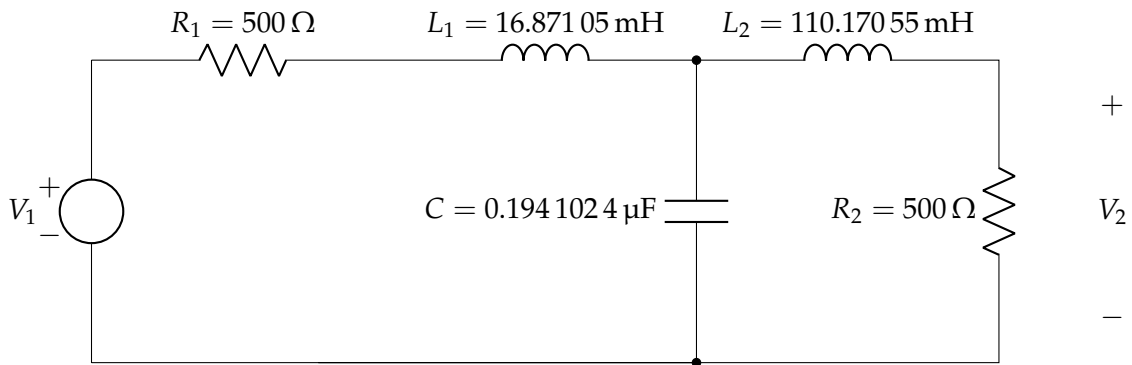


Figure 26: Bessel filter at normalized frequency of 1000 rad/sec

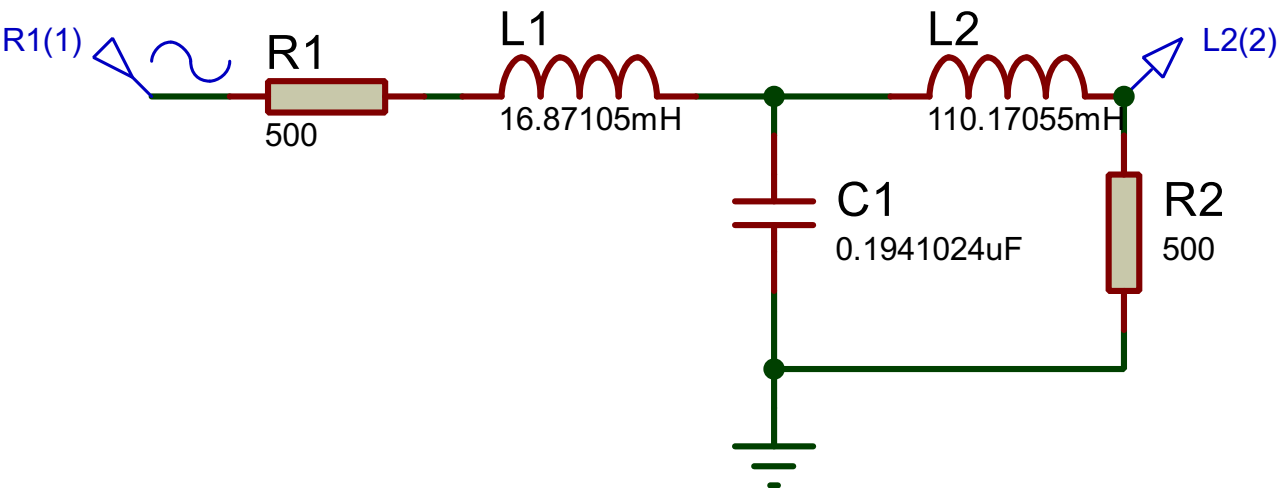


Figure 27: Proteus Circuit Figure d

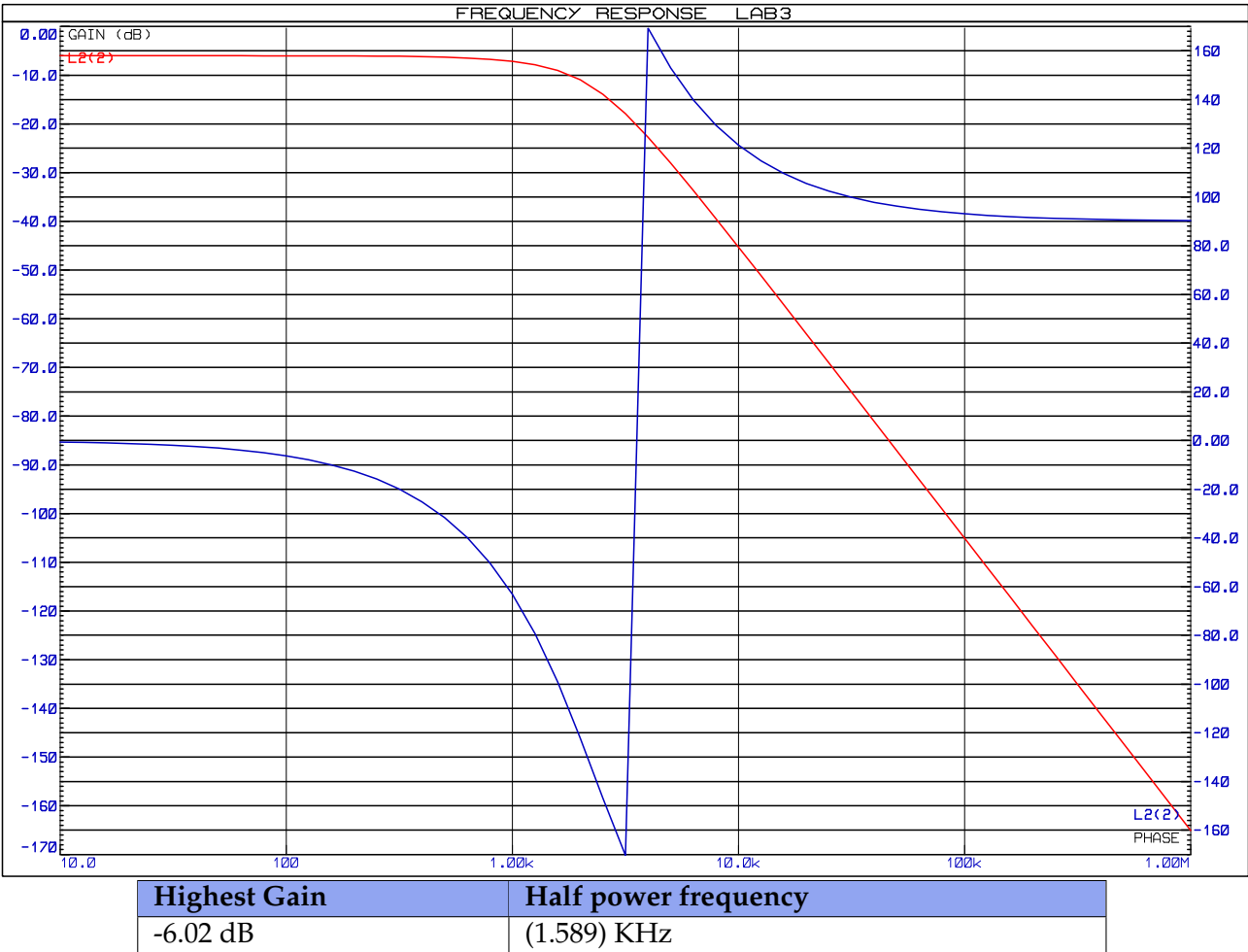


Figure 28: Proteus Observation Figure d

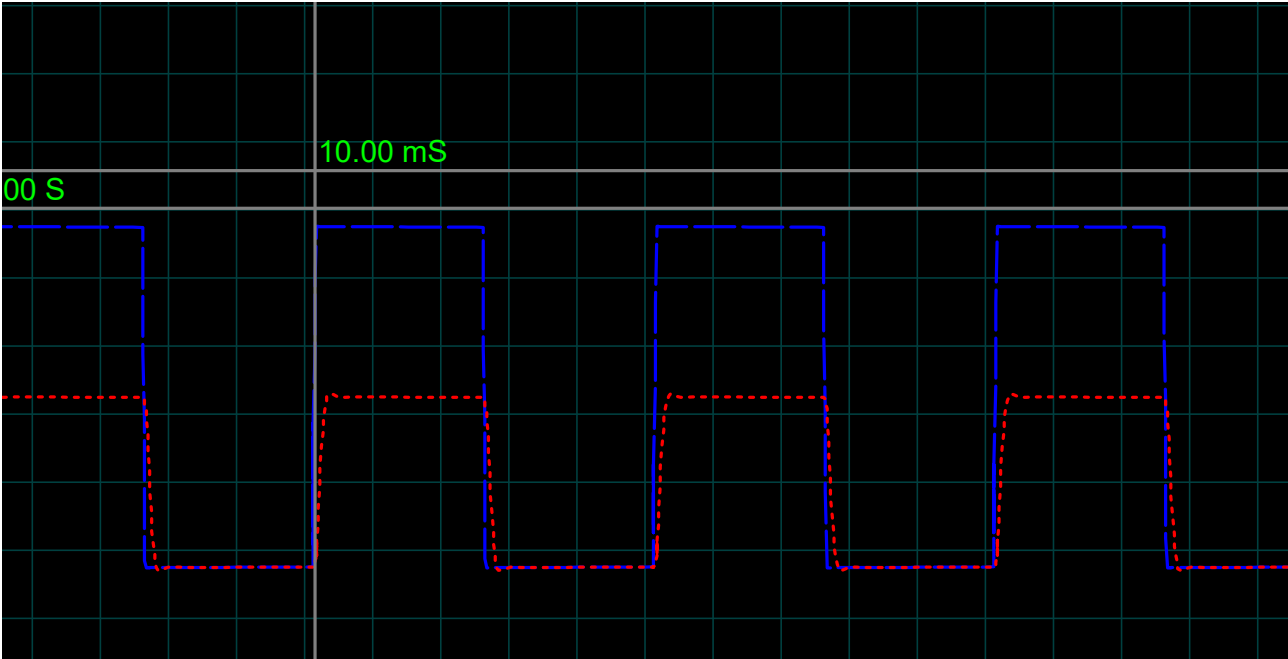


Figure 29: Output signal for input square wave of 100Hz

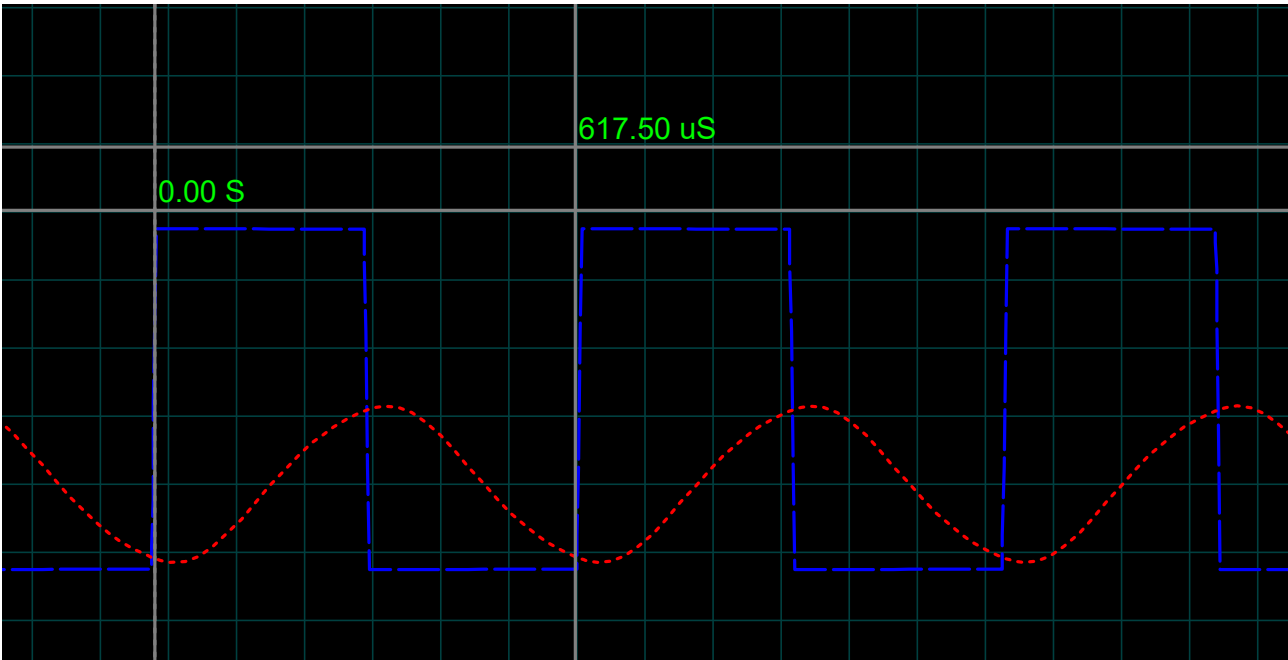


Figure 30: Output signal for input square wave of 1.6kHz

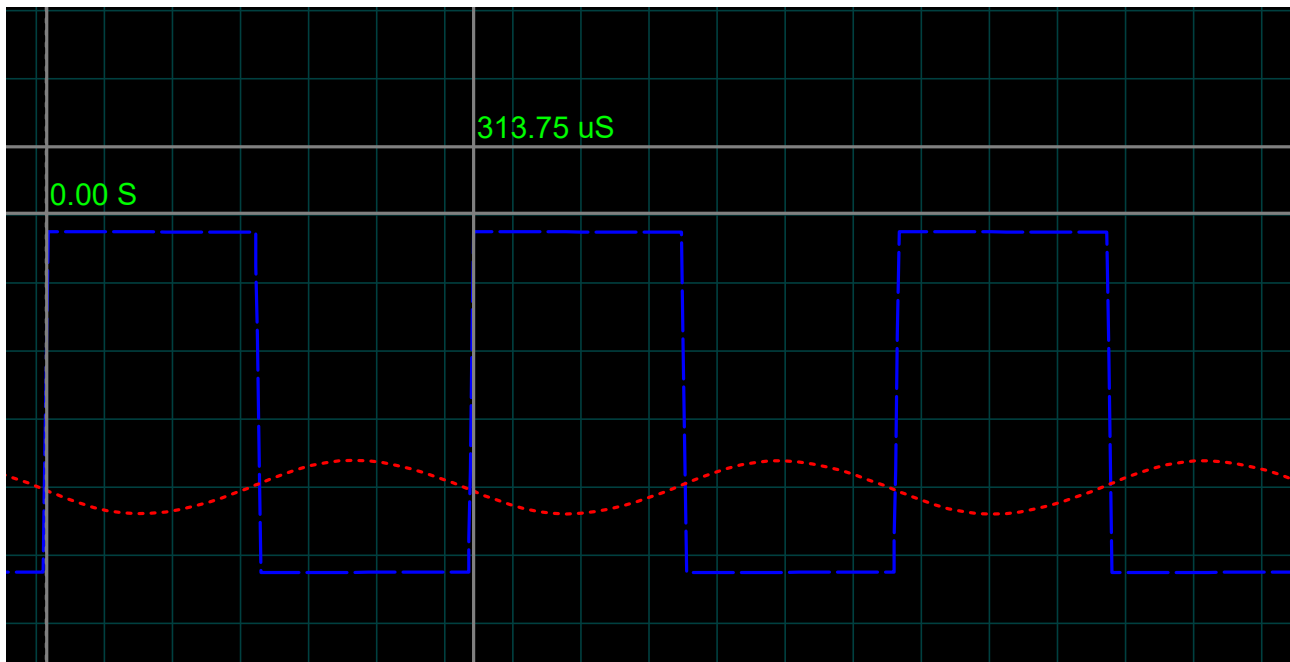


Figure 31: Output signal for input square wave of 3.2kHz

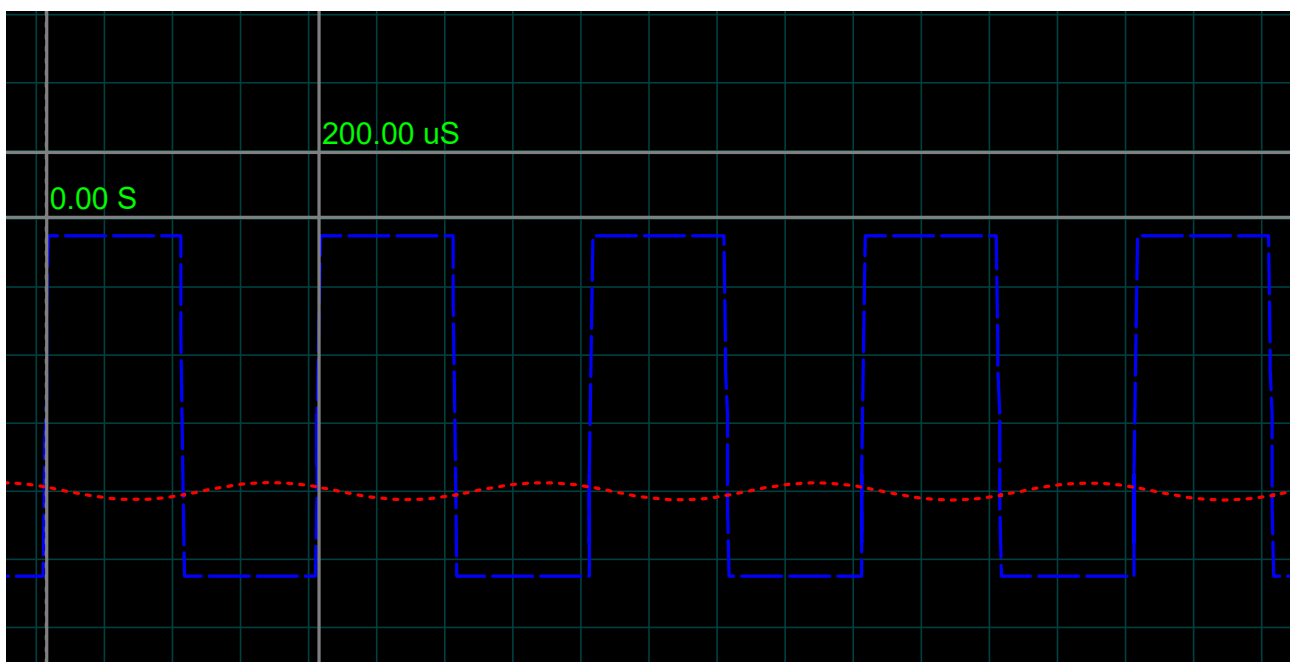


Figure 32: Output signal for input square wave of 5kHz

In above observation , in 100 Hz spikes is seen near the edges . As the frequency increases and reached 1.6kHz sine wave is seen in the middle. From 3.2 khz to 5.0 khz , the output is getting smother.

6 Discussion & Conclusion

In this Lab we did comparison of magnitude & phase response different Filter Networks. We used Proteus design suite to design and plot frequency response for the circuit. We studied and design

practically realizable Butterworth, Chebyshev and Bessel filters. We also derive transfer function for these filters hence fulfilling our objectives of lab.